

Lab1

107060017 廖鳳汝

1.

Design Specification


✓ Input / Output

For a full adder($s+cout=x+y+cin$):

Input: x, y, cin .

Output: $s, cout$.

✓ Block Diagram

 


Design Implementation

✓ Logic Functions


$$s = x \oplus y \oplus cin$$


$$cout = (x \wedge y) \wedge cin \vee x \wedge y$$

✓ Logic Diagram

 

✓ Simulation

 

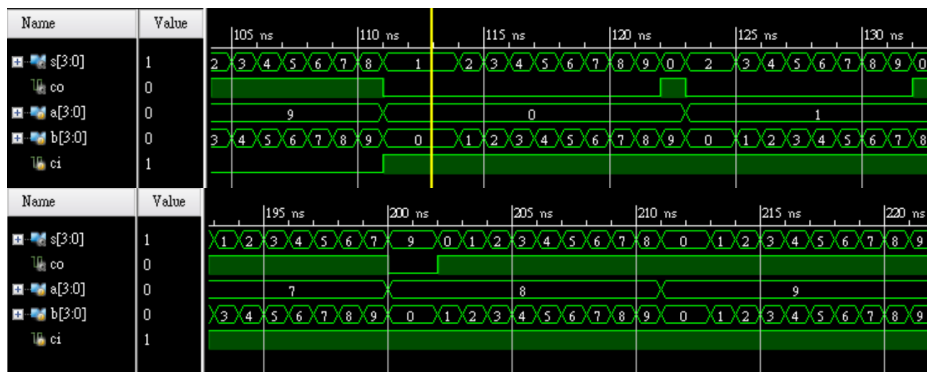

3.

Design Specification


✓ Input / Output

For a 3-to-8-line decoder:

Input: [2:0]in, en

Output: [7:0]d

✓ Block Diagram

 


Design Implementation

✓ Logic Functions


3.1

$$\begin{aligned}
 d[0] &= en \cdot (in[2])' \cdot (in[1])' \cdot (in[0])' \\
 d[1] &= en \cdot (in[2])' \cdot (in[1])' \cdot (in[0]) \\
 d[2] &= en \cdot (in[2])' \cdot (in[1]) \cdot (in[0])' \\
 d[3] &= en \cdot (in[2])' \cdot (in[1]) \cdot (in[0]) \\
 d[4] &= en \cdot (in[2]) \cdot (in[1])' \cdot (in[0])' \\
 d[5] &= en \cdot (in[2]) \cdot (in[1])' \cdot (in[0]) \\
 d[6] &= en \cdot (in[2]) \cdot (in[1]) \cdot (in[0])' \\
 d[7] &= en \cdot (in[2]) \cdot (in[1]) \cdot (in[0])
 \end{aligned}$$

✓ Logic Diagram

 

✓ Simulation

 

Discussion

- ✓ Record the thoughts you have throughout this experiment.

這次的實驗做了Full Adder, MUX, 4 and 5 bit adder和decoder, 馬上強迫我們喚回上學期的記憶! 在實驗的過程, 我又翻了以前的講義, 重新理解這些功能做出來的邏輯原理, 寫成程式模擬出結果, 感覺滿踏實的! 更棒的是, 多bit加法器, 多功器這類寫成logic function 都很麻煩, 但用verilog 只要一個"+", "if" 就完成了!

- ✓ Explains why the results came out as you expected, or the things went wrong if they **did** go wrong.

利用block diagram 再寫出正確的logic function, 照理來說出來的結果就會符合我們的預期。但我這次出錯在第二小題的testbench, 後來發現是我的測資間的間隔太大了, 調小以後就能看到所有的測資了!

- ✓ Analyze and explain the experiment results, including any thoughts, comments, or suggestions related to this experiment.

第一小題的Full adder與第三小題的decoder都像是一個大module裡可以用到的功能，或許以後要用到時可以直接將它加進其中的module中。例如第一題可以作成多bit adder，第二題可以作成mux。而這兩個功能也恰巧出現在第二題實作出來了

Conclusion

在這個實驗中，我學會了如何利用verilog將上學期教的Full Adder, MUX,多bit adder和decoder實作模擬出來，並用testbench將所有可能測資試過一遍，檢查自己的對這個功能的理解與實作有沒有錯。

另外，我體會到verilog的好用之處，例如多bit adder:一個“+”就省去了上學期還要開兩個module的麻煩。