

1.

Design Specification


✓ Input/Output

For a 4-bit synchronous binary up counter:

Input: clk , rst_n .


Output: $q[3:0]$.

✓ Block Diagram

 


Design Implementation

✓ Logic Diagram

 

✓ Simulation

 

2.

Design Specification


✓ Input/Output

For a ring counter of 8 DFFs:

Input: clk, rst_n.

Output: T[7:0].

✓ Block Diagram

 

Design Implementation

✓ Simulation

